

*ELEC0014 - Introduction to power and energy systems*

## Balanced three-phase systems and operation

Thierry Van Cutsem


`t.vancutsem@ulg.ac.be`

`www.montefiore.ulg.ac.be/~vct`

September 2019

- system used for the major part of transmission and distribution of electric energy (except for high-voltage direct current links)
- advantages: saving of conductors, production of rotating magnetic fields in machines
  
- balanced three-phase circuit = an assembly of three identical circuits called *phases*
- balanced three-phase operation: at the corresponding points of the three phases, the voltages (resp. the currents) have the same effective (or RMS) value but are shifted in time by one third of a period from one phase to another.

# Principle

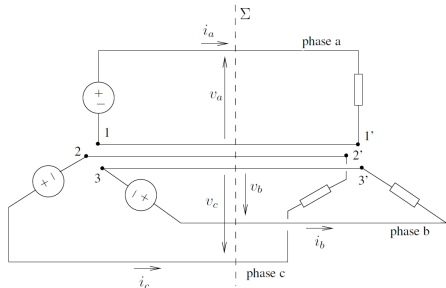

$$v_a(t) = \sqrt{2}V \cos(\omega t + \theta)$$

$$v_b(t) = \sqrt{2}V \cos\left(\omega\left(t - \frac{T}{3}\right) + \theta\right) = \sqrt{2}V \cos\left(\omega t + \theta - \frac{2\pi}{3}\right)$$


$$v_c(t) = \sqrt{2}V \cos\left(\omega\left(t - \frac{2T}{3}\right) + \theta\right) = \sqrt{2}V \cos\left(\omega t + \theta - \frac{4\pi}{3}\right)$$

$$i_a(t) = \sqrt{2}I \cos(\omega t + \psi)$$

$$i_b(t) = \sqrt{2}I \cos\left(\omega\left(t - \frac{T}{3}\right) + \psi\right) = \sqrt{2}I \cos\left(\omega t + \psi - \frac{2\pi}{3}\right)$$

$$i_c(t) = \sqrt{2}I \cos\left(\omega\left(t - \frac{2T}{3}\right) + \psi\right) = \sqrt{2}I \cos\left(\omega t + \psi - \frac{4\pi}{3}\right)$$

# Phasor diagrams

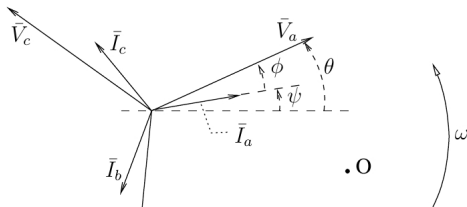

$$\bar{V}_a = V e^{j\theta}$$

$$\bar{V}_b = V e^{j(\theta - \frac{2\pi}{3})} = \bar{V}_a e^{-j\frac{2\pi}{3}}$$

$$\bar{V}_c = V e^{j(\theta - \frac{4\pi}{3})} = \bar{V}_a e^{-j\frac{4\pi}{3}} = \bar{V}_b e^{-j\frac{2\pi}{3}} \quad \Rightarrow \quad \bar{V}_a + \bar{V}_b + \bar{V}_c = 0$$

$$\bar{I}_a = I e^{j\psi}$$

$$\bar{I}_b = I e^{j(\psi - \frac{2\pi}{3})} = \bar{I}_a e^{-j\frac{2\pi}{3}}$$


$$\bar{I}_c = I e^{j(\psi - \frac{4\pi}{3})} = \bar{I}_a e^{-j\frac{4\pi}{3}} = \bar{I}_b e^{-j\frac{2\pi}{3}} \quad \Rightarrow \quad \bar{I}_a + \bar{I}_b + \bar{I}_c = 0$$

An observer located in O sees the rotating vectors passing in the order  $a, b, c$

$\bar{V}_a, \bar{V}_b, \bar{V}_c$  make up a *direct sequence*
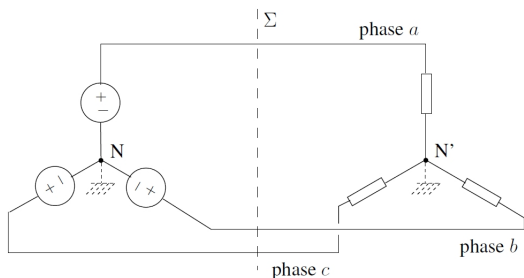
# A more interesting configuration

The return conductors 11', 22' et 33' are merged into a single conductor... which carries a current  $\bar{I}_a + \bar{I}_b + \bar{I}_c = 0$  ... and, hence, is removed




The power through  $\Sigma = 3$  times the power in one phase, using only 1.5 times the number of conductors in one phase.

N, N' : *neutrals*. In balanced three-phase operation, all neutrals are at the same voltage.

$\bar{V}_a, \bar{V}_b, \bar{V}_c$  : *phase or phase-to-neutral or line-to-neutral voltages*
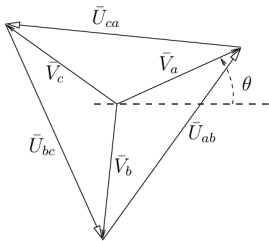
# Line voltages (or voltages between phases)

$$\bar{U}_{ab} = \bar{V}_a - \bar{V}_b \quad \bar{U}_{bc} = \bar{V}_b - \bar{V}_c \quad \bar{U}_{ca} = \bar{V}_c - \bar{V}_a$$




$$\bar{U}_{ab} = \sqrt{3} \bar{V}_a e^{j\frac{\pi}{6}} = \sqrt{3} V e^{j(\theta + \frac{\pi}{6})} \quad \bar{U}_{bc} = \sqrt{3} \bar{V}_b e^{j\frac{\pi}{6}} \quad \bar{U}_{ca} = \sqrt{3} \bar{V}_c e^{j\frac{\pi}{6}}$$

RMS value of line voltage =  $\sqrt{3} \times$  RMS value of phase voltage

$\bar{U}_{ab}$ ,  $\bar{U}_{bc}$  et  $\bar{U}_{ca}$  also make up a direct sequence.

When specifying the voltage at the terminal of a three-phase device, unless otherwise specified, it is the effective (or RMS) value of the line voltages.
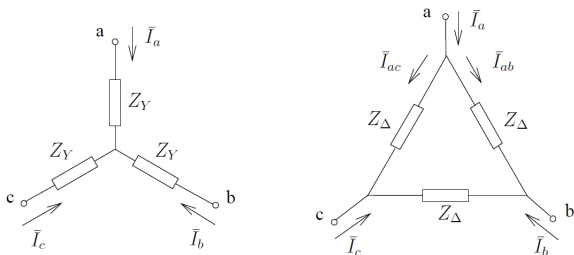
# Star and delta (or triangle) connections



Relation between  $\bar{I}_{ab}$  and  $\bar{I}_a$  in the delta connection ?

$$\bar{I}_a = \frac{\bar{U}_{ab} + \bar{U}_{ac}}{Z_\Delta} = \frac{\bar{U}_{ab} - \bar{U}_{ca}}{Z_\Delta} = \frac{\bar{U}_{ab} - \bar{U}_{ab} e^{-j\frac{4\pi}{3}}}{Z_\Delta} = \frac{\bar{U}_{ab}}{Z_\Delta} (1 - e^{-j\frac{4\pi}{3}}) = \sqrt{3} e^{-j\frac{\pi}{6}} \bar{I}_{ab}$$

If the same voltages  $\bar{V}_a$ ,  $\bar{V}_b$  and  $\bar{V}_c$  are applied to both schemes, the phase currents  $\bar{I}_a$ ,  $\bar{I}_b$  et  $\bar{I}_c$  will be also the same if :  $Z_\Delta = 3 Z_Y$

Exercise. Establish this result by expressing that both circuits consume the same three-phase complex power.

## In practice:

- ① single phase loads are placed in the branches of either stars or deltas, according to the desired voltage
  - example: three-phase power supply at 400 V (between phases): appliances designed to operate under 230 V are placed between one phase and the neutral
- ② at the level of one house:
  - modern distribution: three-phase supply
  - the distribution company provides a neutral conductor
  - the various single-phase loads are connected to the phases so that the latter are balanced as much as possible
  - there remains some phase imbalance → nonzero current in the neutral conductor
- ③ as more and more houses are supplied, the total neutral current becomes negligible compared to the phase currents
- ④ most of the inverters used in residential photovoltaic units are single-phase units; they give rise to imbalances
- ⑤ however, most of the loads seen from the **transmission** network can be considered to be balanced (imbalance cancellation due to large number of individual loads involved).



# Per-phase analysis


Balanced three-phase operation  $\Rightarrow$  consider only one of the three phases.

Voltages and current phasors in the other phases are merely shifted by  $\pm 2\pi/3$  rad.

In order to handle a single phase and discard the other two :

- the delta-connected three-phase loads must be replaced by their star-connected equivalents
- the inductive and capacitive couplings between phases must be taken into account.
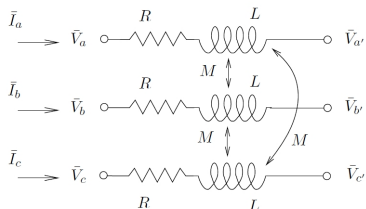
## Handling of inductive couplings between phases



Approximation: assume perfectly balanced couplings:

$$\begin{bmatrix} \bar{V}_a \\ \bar{V}_b \\ \bar{V}_c \end{bmatrix} = \begin{bmatrix} \bar{V}_{a'} \\ \bar{V}_{b'} \\ \bar{V}_{c'} \end{bmatrix} + \begin{bmatrix} Z_s & Z_m & Z_m \\ Z_m & Z_s & Z_m \\ Z_m & Z_m & Z_s \end{bmatrix} \begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix}$$

Developing the first component:


$$\begin{aligned} \bar{V}_a &= \bar{V}_{a'} + Z_s \bar{I}_a + Z_m \bar{I}_b + Z_m \bar{I}_c \\ &= \bar{V}_{a'} + \left[ Z_s + Z_m (e^{-j\frac{2\pi}{3}} + e^{-j\frac{4\pi}{3}}) \right] \bar{I}_a \\ &= \bar{V}_{a'} + [Z_s - Z_m] \bar{I}_a \end{aligned}$$

Thus, phase  $a$  can be considered alone but with a series impedance:

$$Z_{eq} = Z_s - Z_m$$

named *cyclic impedance*.


Example of previous slide:

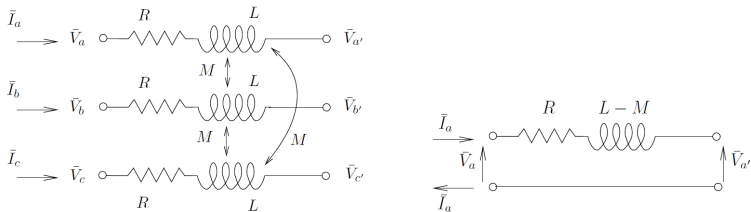

$$Z_{eq} = R + j\omega(L - M)$$

**Remark.** The return conductor is needed to carry the return current in the equivalent circuit; it does not exist in the original three-phase circuit!
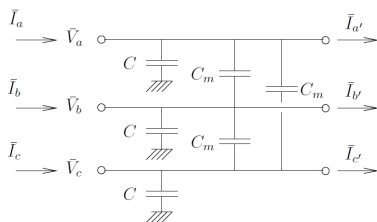
## Handling of capacitive couplings between phases



Approximation: assume perfectly balanced couplings:

$$\begin{bmatrix} \bar{I}_a - \bar{I}_{a'} \\ \bar{I}_b - \bar{I}_{b'} \\ \bar{I}_c - \bar{I}_{c'} \end{bmatrix} = \begin{bmatrix} Y_s & Y_m & Y_m \\ Y_m & Y_s & Y_m \\ Y_m & Y_m & Y_s \end{bmatrix} \begin{bmatrix} \bar{V}_a \\ \bar{V}_b \\ \bar{V}_c \end{bmatrix}$$

Developing the first component:


$$\begin{aligned} \bar{I}_a - \bar{I}_{a'} &= Y_s \bar{V}_a + Y_m \bar{V}_b + Y_m \bar{V}_c \\ &= \left[ Y_s + Y_m (e^{-j\frac{2\pi}{3}} + e^{-j\frac{4\pi}{3}}) \right] \bar{V}_a \\ &= [Y_s - Y_m] \bar{V}_a \end{aligned}$$

Thus, phase  $a$  can be considered alone but with a shunt admittance:

$$Y_{eq} = Y_s - Y_m$$

between phase and neutral.

Example of previous slide:

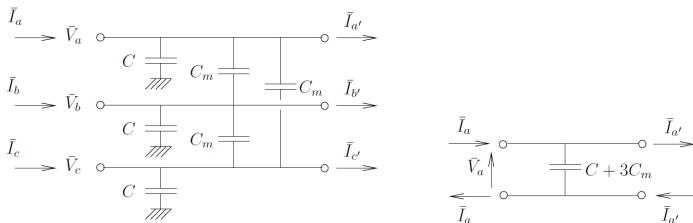


$$Y_s = j\omega C + 2j\omega C_m$$

$$Y_m = -j\omega C_m$$

and hence: 
$$Y_{eq} = j\omega(C + 3C_m)$$
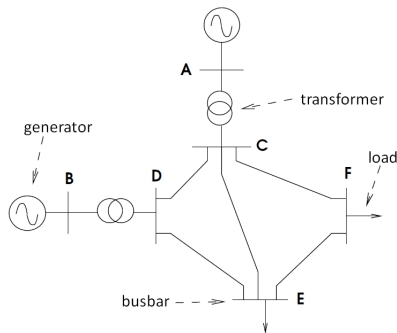
## One-line diagram

Single-phase diagram without return conductor



In the switching stations, lines, cables, transformers, generators, loads, etc. are connected to each other through *buses* or *busbars*<sup>1</sup>

Bus (or busbar) = equipotential metallic assembly

<sup>1</sup>En français, l'ensemble des barres relatives aux trois phases est appelé *jeu de barres*

# Powers in balanced three-phase systems

## Instantaneous power through the section $\Sigma$ :

$$\begin{aligned}
 p(t) &= v_a i_a + v_b i_b + v_c i_c \\
 &= 2VI \left[ \cos(\omega t + \theta) \cos(\omega t + \psi) + \cos\left(\omega t + \theta - \frac{2\pi}{3}\right) \cos\left(\omega t + \psi - \frac{2\pi}{3}\right) \right. \\
 &\quad \left. + \cos\left(\omega t + \theta - \frac{4\pi}{3}\right) \cos\left(\omega t + \psi - \frac{4\pi}{3}\right) \right] \\
 &= 3VI \cos(\theta - \psi) + VI \left[ \cos(2\omega t + \theta + \psi) \right. \\
 &\quad \left. + \cos\left(2\omega t + \theta + \psi - \frac{4\pi}{3}\right) + \cos\left(2\omega t + \theta + \psi - \frac{2\pi}{3}\right) \right] \\
 &= 3VI \cos(\theta - \psi) = 3VI \cos \phi = 3P
 \end{aligned}$$

- no fluctuating power!
- instantaneous power =  $3 \times$  active power transfer  $P$  in one of the phases
- **in each phase there is a fluctuating power.** The magnitude of its component relative to reactive current is the single-phase reactive power  $Q$ .

## Complex three-phase power

By extension of the single-phase formula:

$$\begin{aligned}
 S_{tri} &= \bar{V}_a \bar{I}_a^* + \bar{V}_b \bar{I}_b^* + \bar{V}_c \bar{I}_c^* \\
 &= \bar{V}_a \bar{I}_a^* + \bar{V}_a e^{-j\frac{2\pi}{3}} \bar{I}_a^* e^{j\frac{2\pi}{3}} + \bar{V}_a e^{-j\frac{4\pi}{3}} \bar{I}_a^* e^{j\frac{4\pi}{3}} \\
 &= 3\bar{V}_a \bar{I}_a^*
 \end{aligned}$$

Three-phase active power :  $re(S_{tri}) = P_{tri} = 3VI \cos \phi = 3P$

Three-phase reactive power:  $im(S_{tri}) = Q_{tri} = 3VI \sin \phi = 3Q$

$Q_{tri}$  is an **artificial notion** :

- since there is no three-phase fluctuating power
- only the single-phase reactive power  $Q$  has an interpretation
- it is as artificial as would be a “three-phase current”  $3I$

However, the three-phase reactive power is used worldwide, for its symmetry with the three-phase active power.



## Expressions involving the line voltage

To designate the voltage in a three-phase system, one uses generally:

$$U = \text{effective (or RMS) value of line voltage} = \sqrt{3}V$$

$$P_{tri} = \sqrt{3}UI \cos \phi$$

$$Q_{tri} = \sqrt{3}UI \sin \phi$$

These formulae are “hybrid” in so far as:

- $U$  is the effective value of the *line voltage*
- while  $\phi$  is the phase angle between the line current and the *phase-to-neutral* voltage.